


CPE 487 Midterm Exam (100 Points)

Due: October 18, 12:30pm


Signed \_\_\_\_\_ Date \_\_\_\_\_

**Part1:** By hands only

 - Complete the timing diagram of the following circuit by adding the timing trace for **f** and **g**:



 - Write Boolean expression for the following circuits:




- Draw the logic diagram corresponding to the following Boolean expression:

$$(AB + A'B')(CD' + C'D)$$

## Part 2: Using Vivado

 4. Use Vivado to write VHDL gate-level description encoder circuit shown below



5. Write behavioral (testbench) description of a four-input encoder circuit shown in #4, above.